

1

a

$$V = V_1 + V_2 \Rightarrow I \cdot R_1 = V_1, I \cdot R_2 = V_2$$

$$\hookrightarrow V = I \cdot R_1 + I \cdot R_2 = I(R_1 + R_2)$$

$$\Rightarrow I = \frac{V}{R_1 + R_2}$$

b


$$R_{eq} = R_1 + R_2 = 1.5k\Omega = 1500\Omega$$

$$V_{eq1} = I \cdot R_1 \Rightarrow I = \frac{V}{R_{eq}} = \frac{9}{1500}A$$

$$V_{eq1} = \frac{9}{1500} \cdot 500 = 9 \cdot \frac{1}{3} = 3V$$

$$V_{eq2} = \frac{9}{1500} \cdot 1000 = 9 \cdot \frac{2}{3} = 6V$$

2

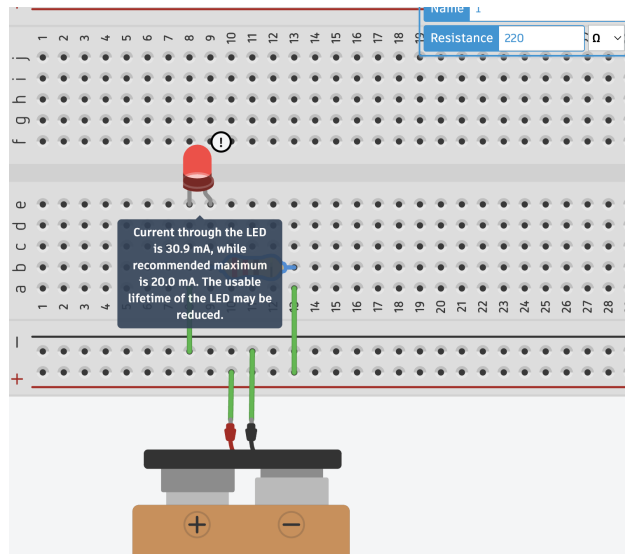

Using KVL:

$$9V - 2V - IR = 0 \Rightarrow I = \frac{7V}{R}$$

- Smaller $R \Rightarrow$ Larger $I \Rightarrow$ Brighter LED
- But $I > 20\text{mA}$ may damage the LED

3

Using Ohm's Law for each branch:

$$I_1 = \frac{V}{R_1} = \frac{9\text{ V}}{900\ \Omega} = 0.01\text{ A}$$

$$I_2 = \frac{V}{R_2} = \frac{9\text{ V}}{450\ \Omega} = 0.02\text{ A}$$

$$I_3 = \frac{V}{R_3} = \frac{9\text{ V}}{450\ \Omega} = 0.02\text{ A}$$

4

$$\frac{1}{R_{eq}} = \frac{R_2 R_3 + R_1 R_3 + R_1 R_2}{R_1 R_2 R_3}$$

$$R_{eq} = \frac{R_1 R_2 R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3}$$


$$\frac{1}{R_{eq}} = \frac{1}{900\ \Omega} + \frac{1}{450\ \Omega} + \frac{1}{450\ \Omega}$$

$$\frac{1}{R_{eq}} = \frac{1}{900\ \Omega} + \frac{2}{900\ \Omega} + \frac{2}{900\ \Omega}$$

$$\frac{1}{R_{eq}} = \frac{1+2+2}{900\ \Omega} = \frac{5}{900\ \Omega}$$

$$R_{eq} = \frac{900\ \Omega}{5} = 180\ \Omega$$

5

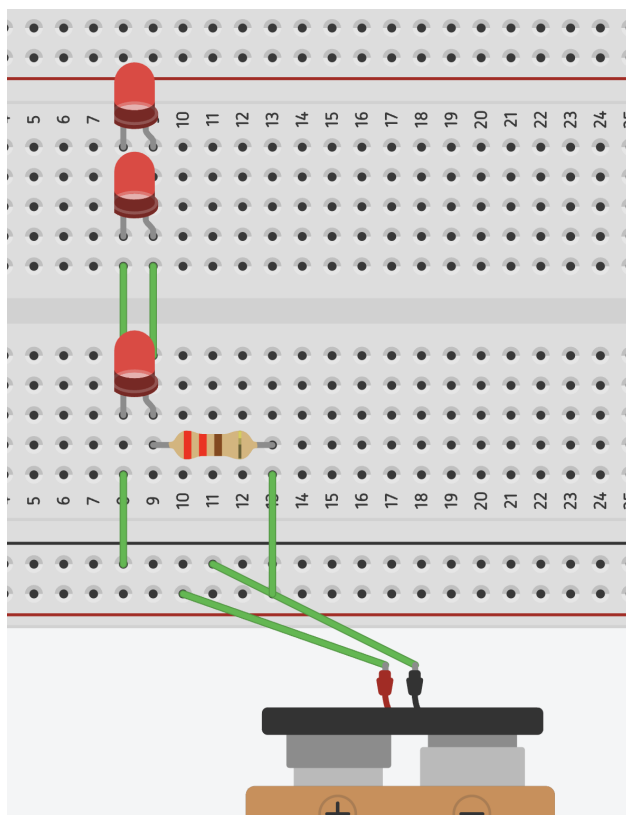

With one LED, the current is $I = (V_{\text{supply}} - V_{\text{LED}})/R = (9\text{ V} - 2\text{ V})/470\ \Omega \approx 14.9\text{ mA}$. With three LEDs in parallel, the total current through R remains 14.9 mA, but by KCL, this current divides among the three LEDs ($\approx 4.96\text{ mA}$ each), causing each LED's brightness to **decrease**.