

1. 12-bit ADC ($V_{ref} = 5\text{ V}$)

- a. Discrete Values:

$$2^{12} = 4096$$

- b. Smallest Voltage Step (Resolution):

$$\frac{5\text{ V}}{2^{12}} = \frac{5\text{ V}}{4096} \approx 0.00122\text{ V} = 1.22\text{ mV}$$

- c. Output for 3.11 V Input:

$$\left(\frac{3.11\text{ V}}{5\text{ V}}\right) \times 4096 = 0.622 \times 4096 \approx 2547.97 \rightarrow \lfloor 2547.97 \rfloor = 2547$$

2. Square Wave

- a. Duty Cycle ($t_{on} = 5\text{ ms}$, $t_{off} = 10\text{ ms}$):

$$T = t_{on} + t_{off} = 5\text{ ms} + 10\text{ ms} = 15\text{ ms}$$



$$\text{Duty Cycle} = \frac{t_{on}}{T} \times 100\% = \frac{5\text{ ms}}{15\text{ ms}} \times 100\% \approx 33.3\%$$


- b. Increasing t_{on} to 10 ms (assuming T changes to 20 ms):

$$\text{New Duty Cycle} = \frac{10\text{ ms}}{20\text{ ms}} \times 100\% = 50\%$$

Effect: LED brightness increases (higher average power).

3. Potentiometer LED Demo

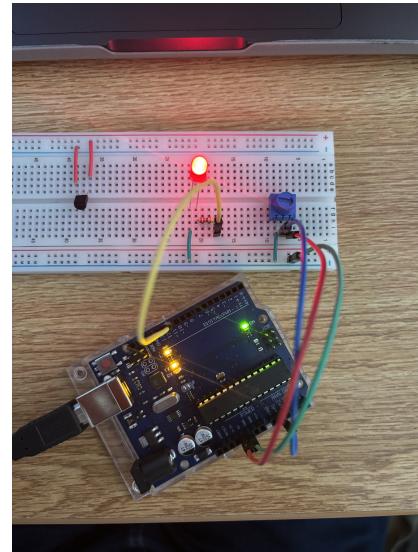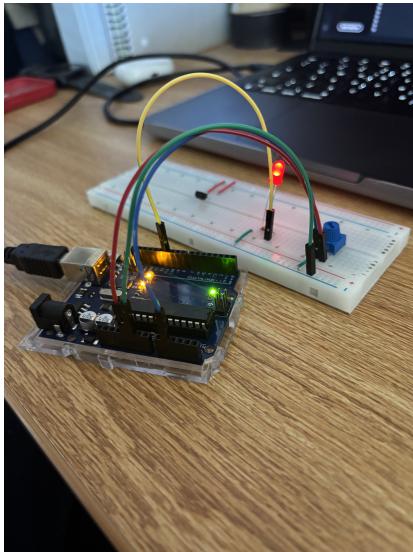

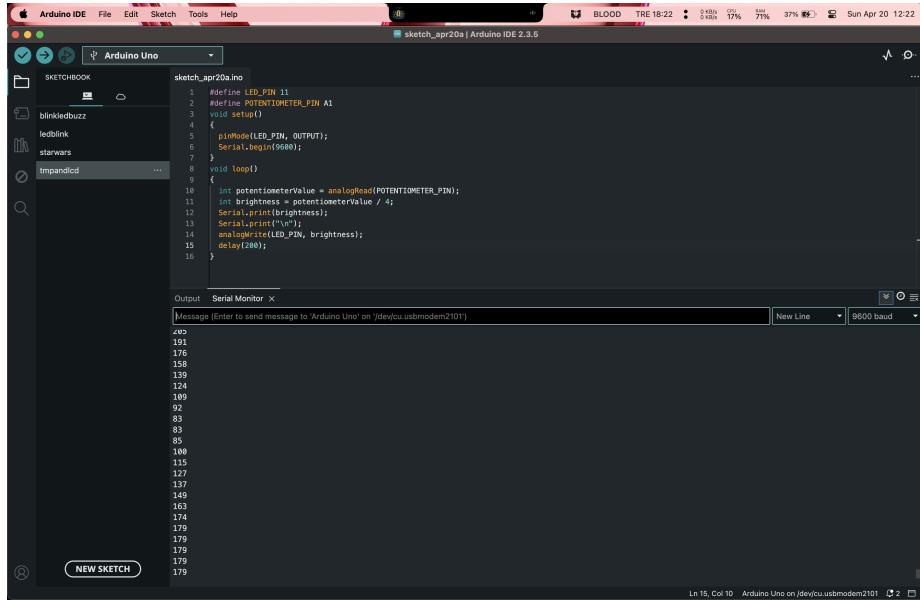

4. TMP36 Reading

$$V_{temp} = V \times (ADC_{in}/1023)$$

$$V_{temp} = 5(205/1023) = 1,0019550342$$

$$t_C = 100 * (V_{temp} - 0.5)$$

$$t_C = 100 * (1.0019550342 - 0.5) = 50,2 C$$

5. Thermistor Circuit

$$V_{A0} = \frac{\text{ADC Reading}}{\text{Total Levels}} \times V_{ref} = \frac{615}{1024} \times 5 \text{ V} \approx 3.003 \text{ V}$$

$$V_{A0} = V_{supply} \times \frac{R}{R_T + R}$$

$$3.003 \text{ V} = 5 \text{ V} \times \frac{10 \text{ k}\Omega}{R_T + 10 \text{ k}\Omega}$$

$$R_T = \left(\frac{V_{supply}}{V_{A0}} - 1 \right) R$$

$$R_T = \left(\frac{5 \text{ V}}{3.003 \text{ V}} - 1 \right) \times 10 \text{ k}\Omega$$

$$R_T \approx (1.665 - 1) \times 10 \text{ k}\Omega \approx 0.665 \times 10 \text{ k}\Omega$$

$$R_T \approx 6.65 \text{ k}\Omega$$

Temperature $\uparrow \implies R_T \downarrow$

R_T will **decrease**.