

Homework 10

EK307

Giacomo Cappelletto

Problem 1:

Solution:

$$\begin{aligned}V_s &= 8\angle -40^\circ \\V_s &= 8 \cos(-40^\circ) + j8 \sin(-40^\circ) = 6.128 - j5.142\text{V} \\|V_s| &= 8.00\text{V}, \quad \angle V_s = -40.0^\circ \\Z_L &= j\omega L = j(2)(3) = j6\Omega \\Z_C &= \frac{1}{j\omega C} = \frac{1}{j(2)(0.25)} = \frac{1}{j0.5} = -j2\Omega \\Z_{R_2C} &= R_2 + Z_C = 2 - j2\Omega \\Z_{\text{parallel}} &= \frac{Z_L \cdot Z_{R_2C}}{Z_L + Z_{R_2C}} = \frac{j6 \cdot (2 - j2)}{j6 + 2 - j2} \\&= \frac{j12 + 12}{2 + j4} = \frac{12 + j12}{2 + j4} \\&= \frac{(12 + j12)(2 - j4)}{(2 + j4)(2 - j4)} = \frac{24 - j48 + j24 + 48}{4 + 16} = \frac{72 - j24}{20} \\Z_{\text{parallel}} &= 3.6 - j1.2\Omega \\|Z_{\text{parallel}}| &= 3.795\Omega, \quad \angle Z_{\text{parallel}} = -18.43^\circ \\Z_{\text{total}} &= R_1 + Z_{\text{parallel}} = 1 + 3.6 - j1.2 = 4.6 - j1.2\Omega \\|Z_{\text{total}}| &= 4.754\Omega, \quad \angle Z_{\text{total}} = -14.62^\circ \\I_s &= \frac{V_s}{Z_{\text{total}}} = \frac{6.128 - j5.142}{4.6 - j1.2} \\&= 1.520 - j0.721\text{A} \\|I_s| &= 1.683\text{A}, \quad \angle I_s = -25.38^\circ \\V_{R_1} &= I_s \cdot R_1 = (1.520 - j0.721)(1) = 1.520 - j0.721\text{V} \\|V_{R_1}| &= 1.683\text{V}, \quad \angle V_{R_1} = -25.38^\circ \\V_{\text{par}} &= V_s - V_{R_1} = (6.128 - j5.142) - (1.520 - j0.721) \\&= 4.608 - j4.421\text{V} \\|V_{\text{par}}| &= 6.386\text{V}, \quad \angle V_{\text{par}} = -43.81^\circ \\I_L &= \frac{V_{\text{par}}}{Z_L} = \frac{4.608 - j4.421}{j6} = -0.737 - j0.768\text{A} \\|I_L| &= 1.064\text{A}, \quad \angle I_L = -133.81^\circ \\I_{R_2C} &= \frac{V_{\text{par}}}{R_2 + Z_C} = \frac{4.608 - j4.421}{2 - j2} \\&= 2.257 + j0.047\text{A} \\|I_{R_2C}| &= 2.258\text{A}, \quad \angle I_{R_2C} = 1.19^\circ\end{aligned}$$

$$V_{R_2} = I_{R_2C} \cdot R_2 = (2.257 + j0.047)(2) = 4.514 + j0.093V$$

$$|V_{R_2}| = 4.515V, \quad \angle V_{R_2} = 1.19^\circ$$

$$V_C = I_{R_2C} \cdot Z_C = (2.257 + j0.047)(-j2) = 0.093 - j4.514V$$

$$|V_C| = 4.515V, \quad \angle V_C = -88.81^\circ$$

$$P_{R_1} = \frac{1}{2} |V_{R_1}|^2 \frac{1}{R_1} = \frac{1}{2} \frac{(1.683)^2}{1} = 1.416W$$

$$P_{R_2} = \frac{1}{2} |V_{R_2}|^2 \frac{1}{R_2} = \frac{1}{2} \frac{(4.515)^2}{2} = 5.097W$$

$$P_L = 0W \quad (\text{reactive element})$$

$$P_C = 0W \quad (\text{reactive element})$$

$$\boxed{P_{R_1} = 1.416 \text{ W}} \quad \boxed{P_{R_2} = 5.097 \text{ W}} \quad \boxed{P_L = 0 \text{ W}} \quad \boxed{P_C = 0 \text{ W}}$$

Problem 2:

Solution:

$$Z_{5 \parallel L} = \frac{R_5 \cdot Z_L}{R_5 + Z_L} = \frac{5 \cdot j2}{5 + j2}$$

$$= \frac{j10}{5 + j2} = \frac{j10(5 - j2)}{(5 + j2)(5 - j2)} = \frac{j50 + 20}{25 + 4} = \frac{20 + j50}{29}$$

$$Z_{5 \parallel L} = 0.6897 + j1.7241\Omega$$

$$Z_{\text{series}} = Z_C + Z_{5 \parallel L} = -j3 + 0.6897 + j1.7241$$

$$Z_{\text{series}} = 0.6897 - j1.2759\Omega$$

$$Z_{\text{th}} = R_4 \parallel Z_{\text{series}} = \frac{4 \cdot (0.6897 - j1.2759)}{4 + 0.6897 - j1.2759}$$

$$= \frac{2.7586 - j5.1034}{4.6897 - j1.2759}$$

$$= \frac{(2.7586 - j5.1034)(4.6897 + j1.2759)}{(4.6897 - j1.2759)(4.6897 + j1.2759)}$$

$$= \frac{12.9383 + j3.5205 - j23.9369 + 6.5119}{22.0013 + 1.6279}$$

$$= \frac{19.4502 - j20.4164}{23.6292}$$

$$Z_{\text{th}} = 0.8234 - j0.8642\Omega$$

$$|Z_{\text{th}}| = 1.194\Omega, \quad \angle Z_{\text{th}} = -46.39^\circ$$

$$\text{Node B: } \frac{V_B - V_s}{R_4} + \frac{V_B - V_C}{Z_C} = 0$$

$$\text{Node C: } \frac{V_C - V_s}{Z_L} + \frac{V_C - V_B}{Z_C} + \frac{V_C}{R_5} = 0$$

$$V_B \left(\frac{1}{R_4} + \frac{1}{Z_C} \right) - V_C \left(\frac{1}{Z_C} \right) = \frac{V_s}{R_4}$$

$$-V_B \left(\frac{1}{Z_C} \right) + V_C \left(\frac{1}{Z_L} + \frac{1}{Z_C} + \frac{1}{R_5} \right) = \frac{V_s}{Z_L}$$

$$a_{11} = \frac{1}{4} + \frac{1}{-j3} = 0.25 + j0.3333$$

$$\begin{aligned}
a_{12} &= -\frac{1}{-j3} = -j0.3333 \\
a_{21} &= -\frac{1}{-j3} = -j0.3333 \\
a_{22} &= \frac{1}{j2} + \frac{1}{-j3} + \frac{1}{5} = -j0.5 + j0.3333 + 0.2 = 0.2 - j0.1667 \\
b_1 &= \frac{165}{4} = 41.25 \\
b_2 &= \frac{165}{j2} = -j82.5 \\
\det &= a_{11}a_{22} - a_{12}a_{21} = (0.25 + j0.3333)(0.2 - j0.1667) - (-j0.3333)(-j0.3333) \\
&= 0.05 - j0.0417 + j0.0667 + 0.0556 - 0.1111 \\
&= -0.0056 + j0.025 \\
V_B &= \frac{b_1a_{22} - b_2a_{12}}{\det} = \frac{41.25(0.2 - j0.1667) - (-j82.5)(-j0.3333)}{-0.0056 + j0.025} \\
&= \frac{8.25 - j6.875 - 27.5}{-0.0056 + j0.025} = \frac{-19.25 - j6.875}{-0.0056 + j0.025} \\
&= \frac{(-19.25 - j6.875)(-0.0056 - j0.025)}{(-0.0056 + j0.025)(-0.0056 - j0.025)} \\
&= \frac{0.1078 + j0.4813 + j0.0385 - 0.1719}{0.0000314 + 0.000625} \\
&= \frac{-0.0641 + j0.5198}{0.0006564} \\
V_{th} &= V_B = 159.22 - j50.10V \\
|V_{th}| &= 166.92V, \quad \angle V_{th} = -17.47^\circ \\
Z_L^{opt} &= Z_{th}^* = 0.8234 + j0.8642\Omega \\
R_{th} &= 0.8234\Omega, \quad X_{th} = -0.8642\Omega \\
P_{max} &= |V_{th}|^2 \frac{1}{4R_{th}} = \frac{(166.92)^2}{4 \cdot 0.8234} \\
P_{max} &= \frac{27860.95}{3.2935} = 8459.54W \\
\boxed{Z_L^{opt} = 0.823 + j0.864 \Omega} \quad \boxed{P_{max} = 8459.5 W}
\end{aligned}$$

Problem 3:

3.a)

Solution:

$$\begin{aligned}
H_{L(s)} &= \frac{V_{o(s)}}{V_{i(s)}} = \frac{sL}{R+sL} \\
H_{L(j\omega)} &= \frac{j\omega L}{R+j\omega L} \\
|H_{L(j\omega)}| &= \frac{\omega L}{\sqrt{R^2 + (\omega L)^2}}
\end{aligned}$$

Low: $\omega \rightarrow 0 \Rightarrow |H_L| \rightarrow 0$

High: $\omega \rightarrow \infty \Rightarrow |H_L| \rightarrow 1$

$$\omega_c = \frac{R}{L} = \frac{200}{0.1} = 2000 \text{ rad/s}$$

$$f_c = \frac{\omega_c}{2\pi} = \frac{2000}{2\pi} \approx 3.18 \times 10^2 \text{ Hz}$$

Filter type: high-pass.

3.b)

Solution:

$$H_{R(s)} = \frac{V_o(s)}{V_i(s)} = \frac{R}{R+sL}$$

$$H_{R(j\omega)} = \frac{R}{R+j\omega L}$$

$$|H_{R(j\omega)}| = \frac{R}{\sqrt{R^2 + (\omega L)^2}}$$

Low: $\omega \rightarrow 0 \Rightarrow |H_R| \rightarrow 1$


High: $\omega \rightarrow \infty \Rightarrow |H_R| \rightarrow 0$

At $\omega = \omega_c$: $|H_R| = \frac{1}{\sqrt{2}} \approx -3 \text{ dB}$

Filter type: low-pass.

3.c)

Solution:

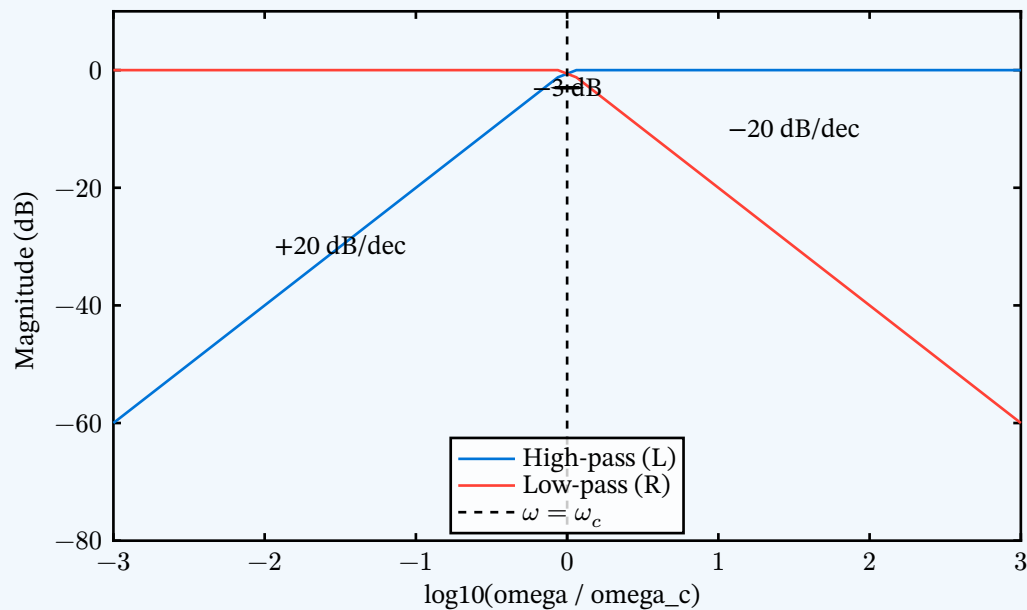

3.d)

Solution:

For RC low-pass: $\omega_c = \frac{1}{R_{\{RC\}}C}$

$$C = \frac{1}{R_{\{RC\}}\omega_c} = \frac{1}{(10^4)(2000)} = 5 \times 10^{-8} \text{ F} = 50 \text{ nF}$$

Circuit: series $10\text{k}\Omega$ from v_i to node, capacitor $C = 50 \text{ nF}$ from node to ground, v_o across C .

Problem 4:

4.a)

Solution:

$$Z_L = j\omega L$$

$$Z_C = \frac{1}{j\omega C}$$

$$Z_R = R$$

$$Z_{\{RC\}} = \left(\frac{1}{R} + j\omega C\right)^{-1}$$

$$H(j\omega) = \frac{V_o}{V_i} = \frac{Z_{\{RC\}}}{Z_L + Z_{\{RC\}}} = \frac{\frac{1}{\frac{1}{R} + j\omega C}}{j\omega L + \frac{1}{\frac{1}{R} + j\omega C}}$$

$$H(j\omega) = \frac{1}{1 + j\omega L \left(\frac{1}{R} + j\omega C\right)}$$

$$j\omega L \left(\frac{1}{R} + j\omega C\right) = j\omega \frac{L}{R} + j^2 \omega^2 LC = j\omega \frac{L}{R} - \omega^2 LC$$

$$H(j\omega) = \frac{1}{1 - \omega^2 LC + j\omega \frac{L}{R}}$$

$$\lim_{\omega \rightarrow 0} |H(j\omega)| = \frac{1}{|1|} = 1$$

$$\lim_{\omega \rightarrow \infty} |H(j\omega)| = \lim_{\omega \rightarrow \infty} \frac{1}{\sqrt{(1 - \omega^2 LC)^2 + \left(\omega \frac{L}{R}\right)^2}} = 0$$

∴ Low-pass filter.

4.b)

Solution:

$$L = 1, \quad C = 1, \quad R = 0.25$$

$$LC = 1$$

$$\frac{L}{R} = 4$$

$$H(j\omega) = \frac{1}{1 - \omega^2 + j4\omega}$$

$$a(\omega) = 1 - \omega^2$$

$$b(\omega) = 4\omega \text{ for } H(\omega) = \frac{1}{a(\omega) + jb(\omega)}$$

Problem 5:

Solution:

$$\omega = 4$$

$$Z_L = j4$$

$$Z_C = \frac{1}{j4 \cdot (0.25)} = -j$$

$$Z_R = 1$$

$$Z_{CR} = 1 - j$$

$$I_{CR} = \frac{V_A}{Z_{CR}}$$

$$I_x = I_L$$

$$I_{\{CR\}} - 0.5I_x - I_x = 0$$

$$I_{\{CR\}} = 1.5I_x$$

$$V_A = V_s - I_x Z_L$$

$$V_A = 1.5I_x Z_{CR}$$

$$I_x(j4 + 1.5(1 - j)) = 24\angle 45^\circ$$

$$I_x = \frac{24\angle 45^\circ}{j4 + 1.5 - 1.5j}$$

$$I_x = 8.23\angle(-14^\circ)$$

$$I_{CR} = 1.5I_x = 12.35\angle(-14^\circ)$$

$$V_o = I_{CR}$$

$$v_{o(t)} = 12.35 \cos(4t - 14^\circ)$$

End of Homework 10